

## Wiring Instructions (TTP223B Touch Sensor to Arduino Uno)

To connect a standard TTP223 capacitive touch sensor to your Arduino Uno, you only need three jumper wires:

- **VCC (Power):** Connect the VCC pin on the touch sensor to the **5V** pin on the Arduino Uno. *(Note: The 3.3V pin will also work, as the TTP223 operates safely between 2V and 5.5V).*
- **GND (Ground):** Connect the GND pin on the touch sensor to any of the **GND** pins on the Arduino Uno.
- **OUT / SIG (Signal):** Connect the OUT (sometimes labeled SIG or I/O) pin on the touch sensor to **Digital Pin 2** on the Arduino Uno.

### How to view the output:

1. Upload the code to your Arduino Uno.
2. Click on the **magnifying glass icon** in the top right corner of the Arduino IDE, or go to **Tools > Serial Monitor**.
3. Ensure the baud rate dropdown in the bottom right corner of the Serial Monitor window is set to **9600 baud** so it matches the `Serial.begin(9600);` line in the setup.